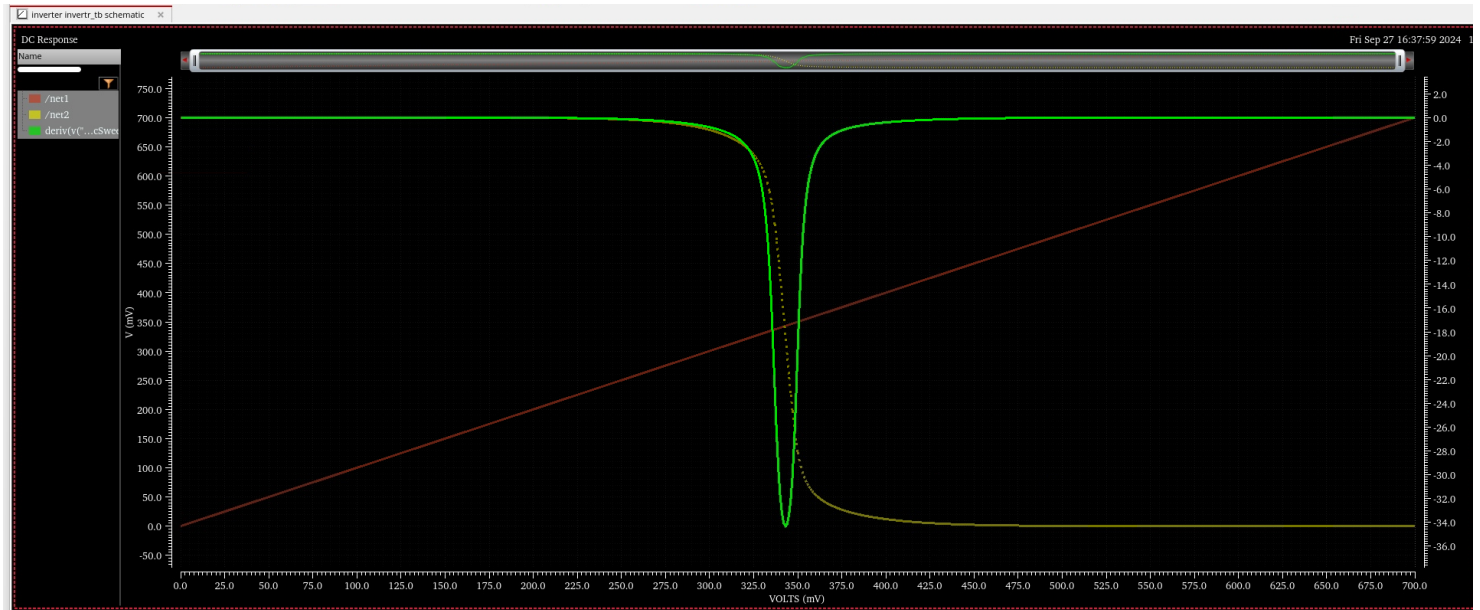



## 1) INVERTER



Gain at  $V_{in} = V_{out}$  is -34.324

Threshold voltage 342.6 mV


## 2) NAND

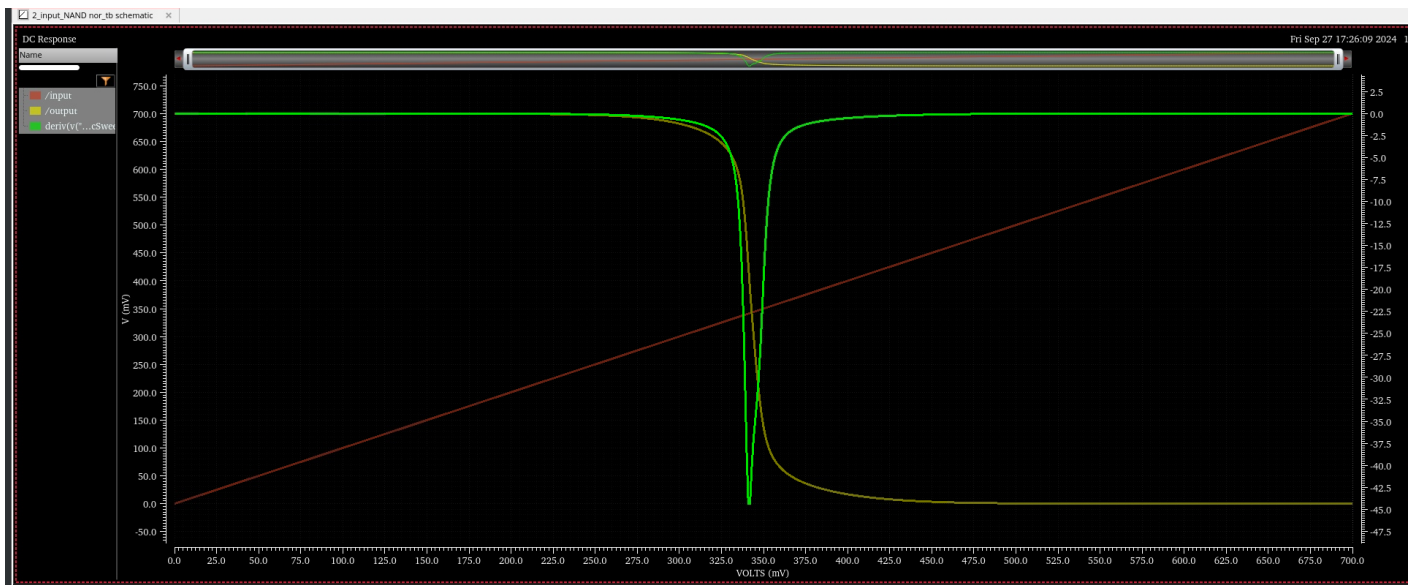

Gain at  $V_{in} = V_{out}$  is -33.792

Threshold voltage = 348.6 mV

### 3) 3 input nor

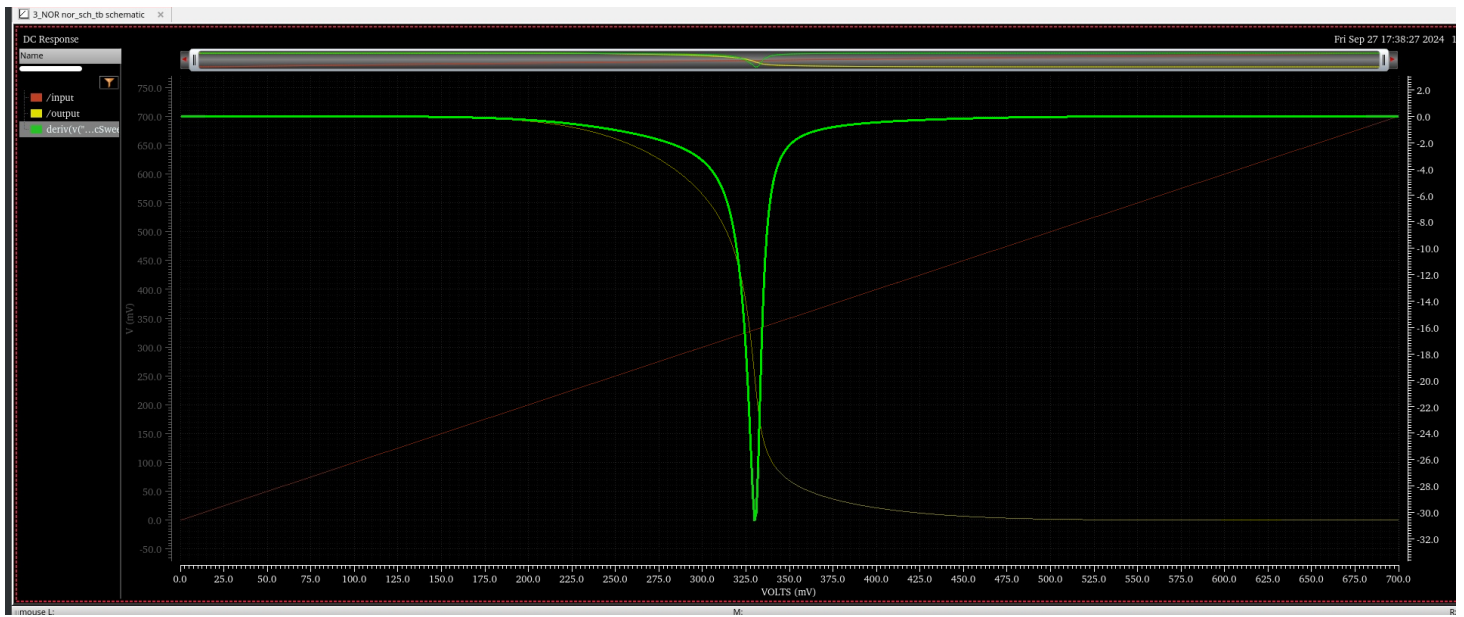


Gain = -55.6


Threshold voltage = 343.2 mV

#### 4) SRAM


a)

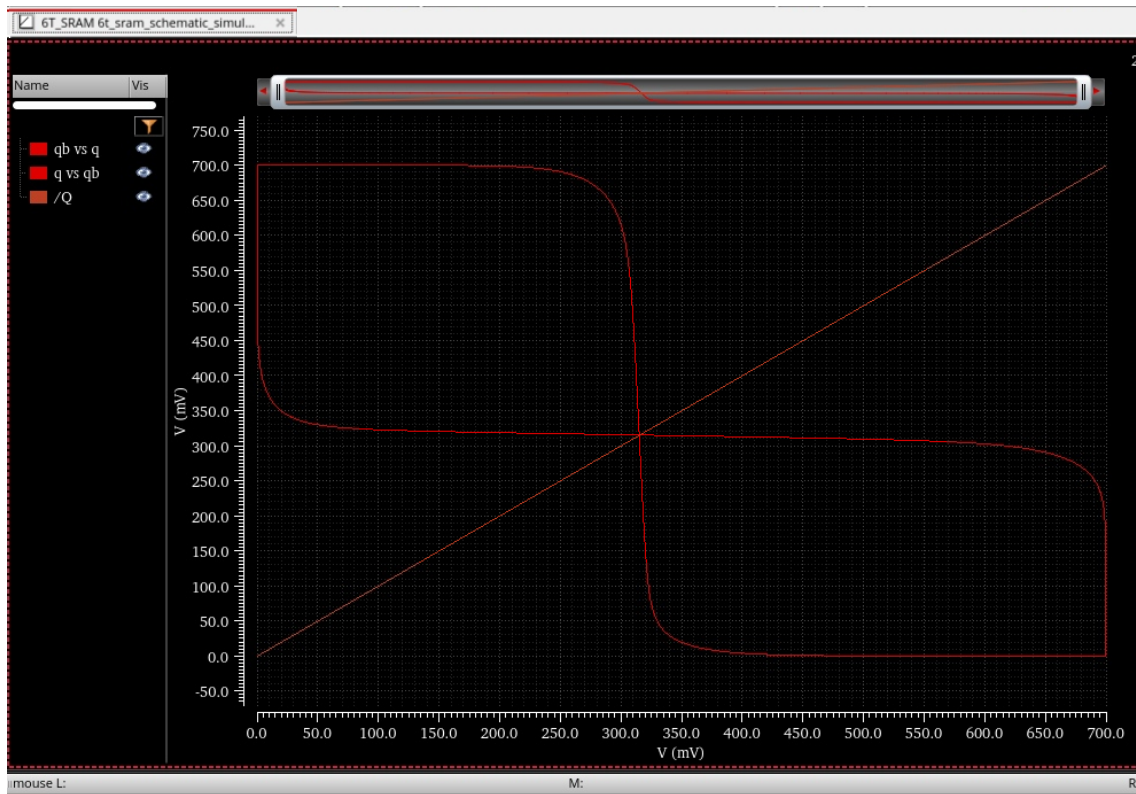


b)

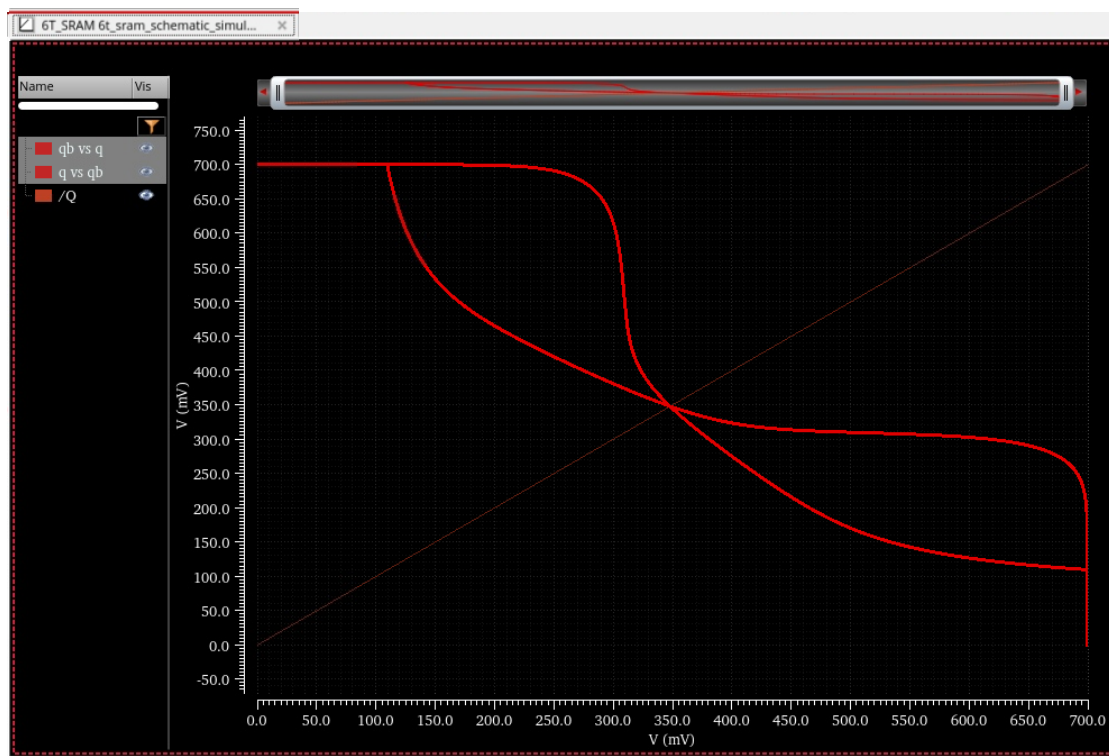

c)

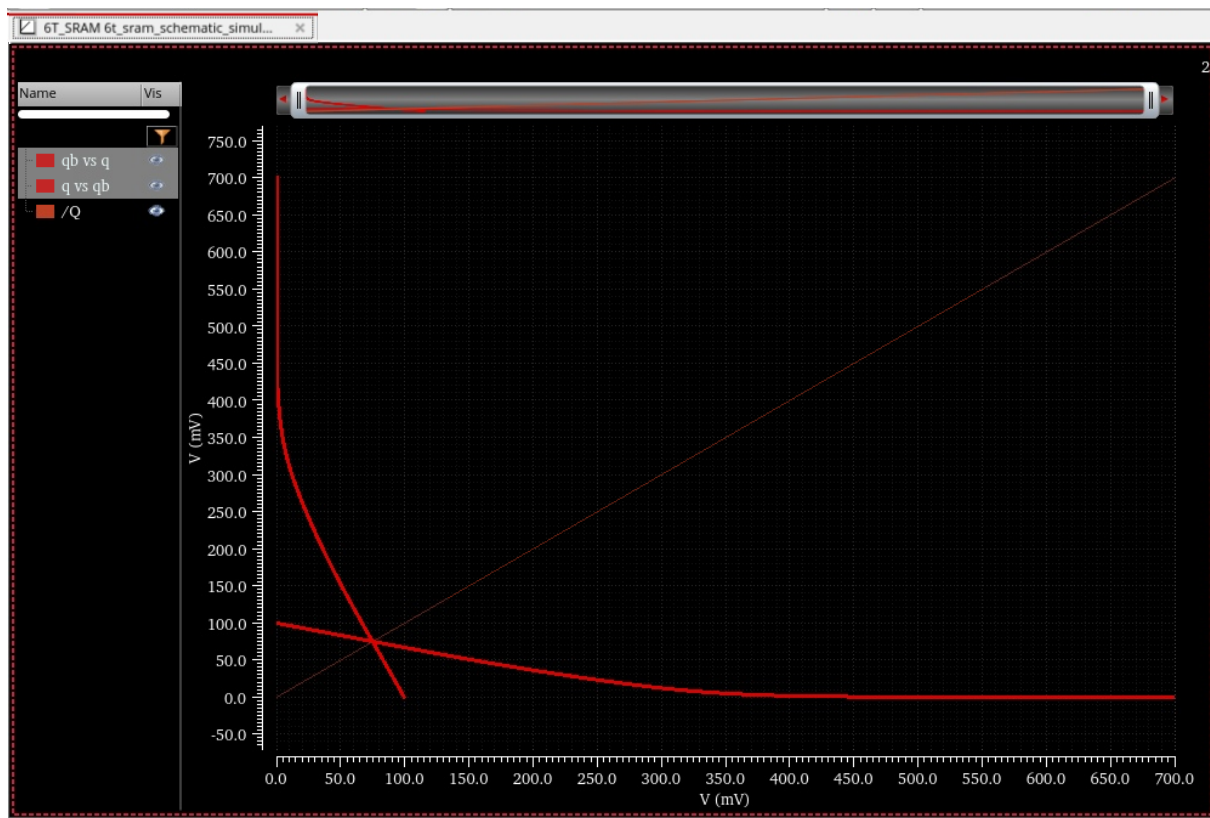


## 5) 4X1 MUX

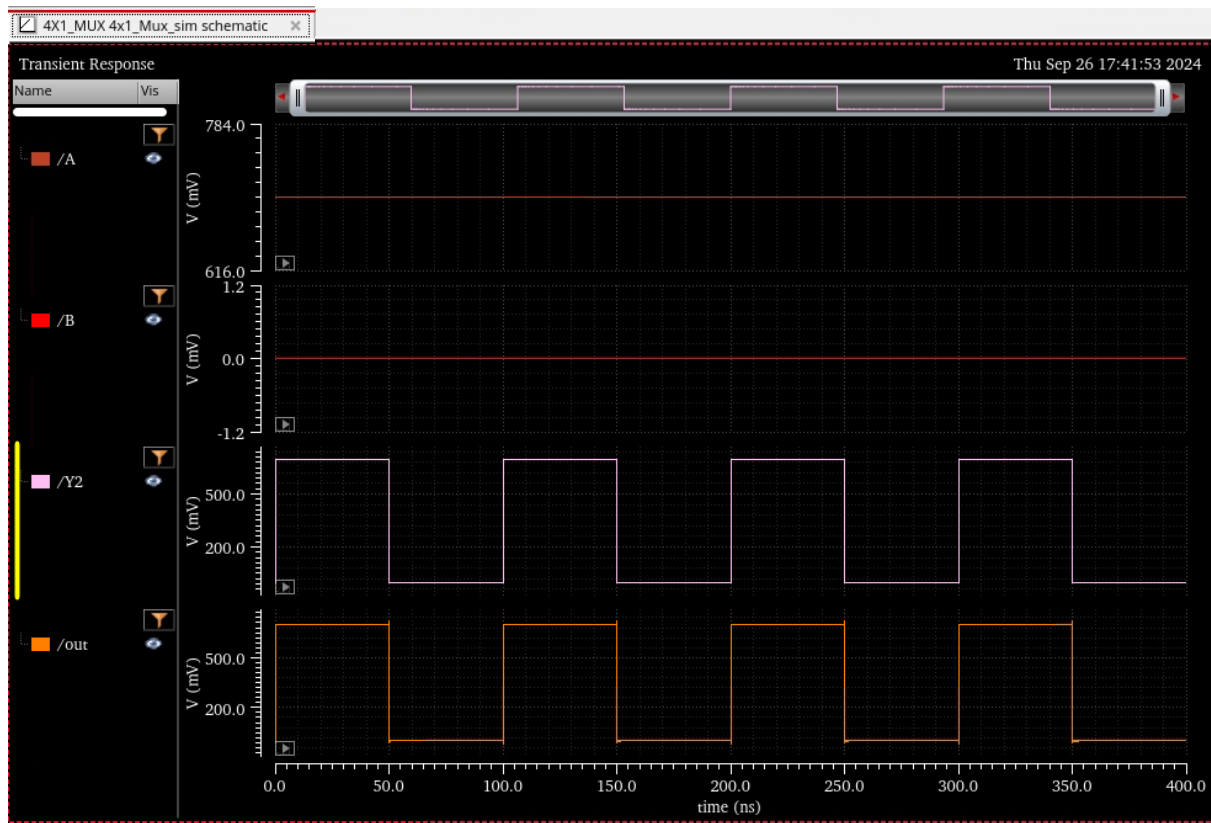

Delay (edge1: rising and edge2: falling) : 52.11E-9

Delay (edge1: falling and edge2: rising) : -47.39E-9

## 6) 2x4 DECODER

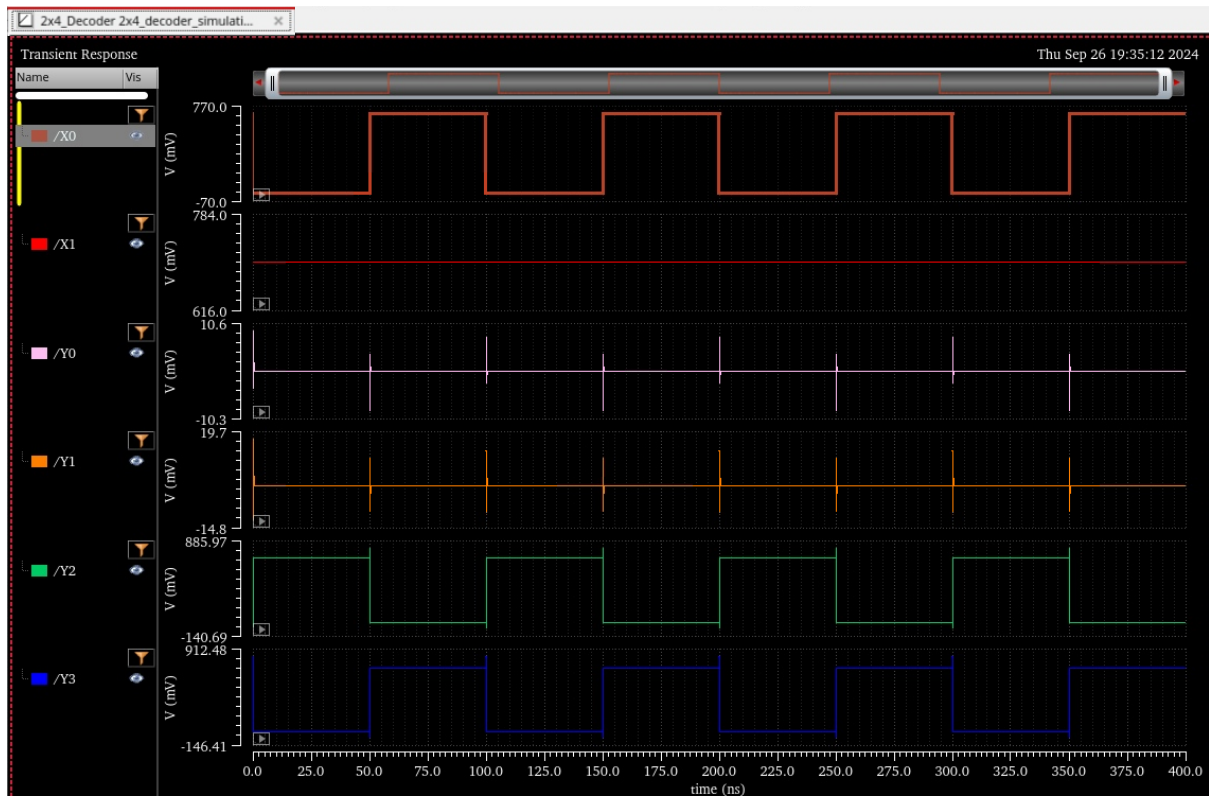

Y3 and Y2 are the only outputs that changes with X0


Delay for Y2: Edge type1 rising: 7.221E-12

: Edge type1 falling: 9.354E-12

Delay for Y3: Edge type1 rising: -50.8E-9

: Edge type1 falling: 50.15E-9

## 7) FULL ADDER

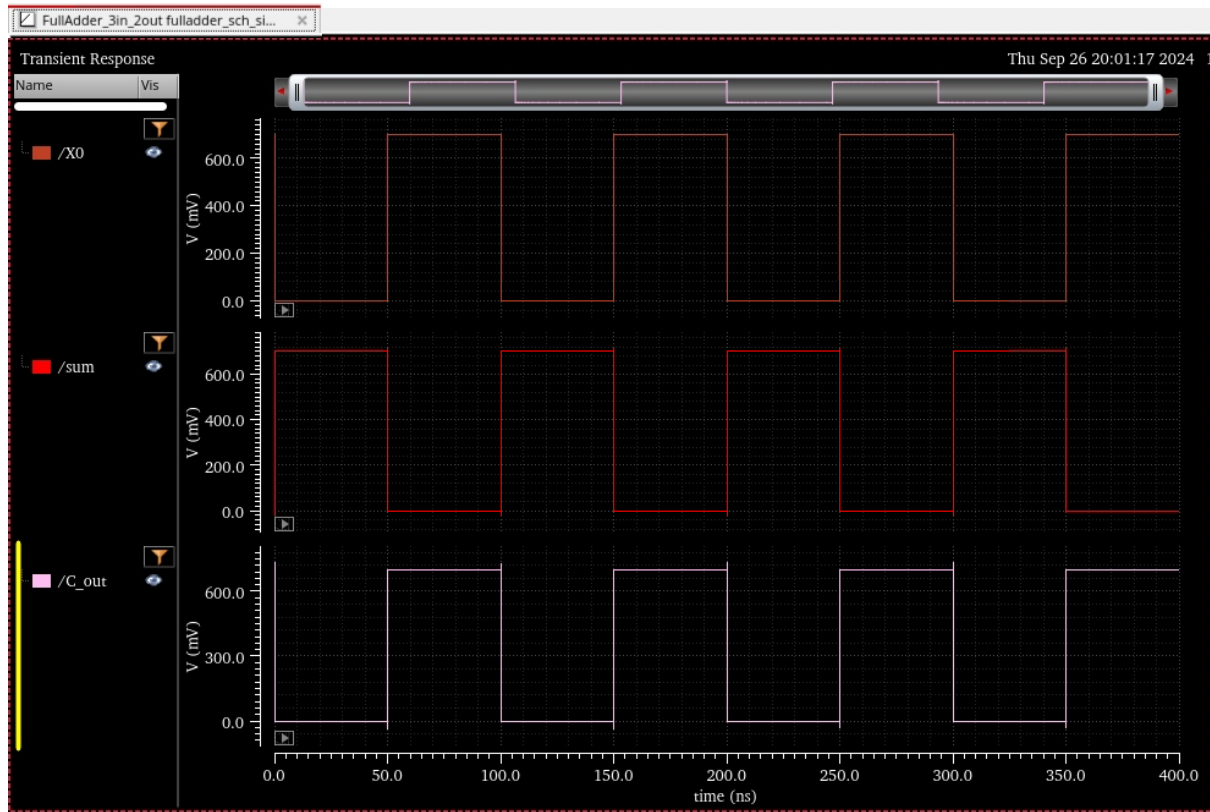

Delay for sum: Edge type1 rising:  $27.68 \times 10^{-12}$

: Edge type1 falling:  $21.76 \times 10^{-12}$

Delay for Co: Edge type1 rising:  $-49.86 \times 10^{-9}$

: Edge type1 falling:  $51.22 \times 10^{-9}$